

# CO002

# Computer Hardware

# Experiment

## Lecture 08: Finite State Machine

Liang Yanyan

澳門科技大學

Macau of University of Science and Technology

# Finite State Machine (FSM)


- A finite state machine has
  - A set of inputs
  - A set of outputs
  - A set of states
  - A function that maps states and inputs to outputs
  - A function that maps states and inputs to states -> state transition function
  - A description of the initial state
- FSM is very useful in designing certain types of systems, e.g. controller.

# Control FSM of R-type

- R-type
  - Instruction fetch
  - Instruction decode, load register
  - Execute
  - Write back result to register
- Can we design a finite state machine representing these states? And output different control signal at different states to control the operation of datapath?
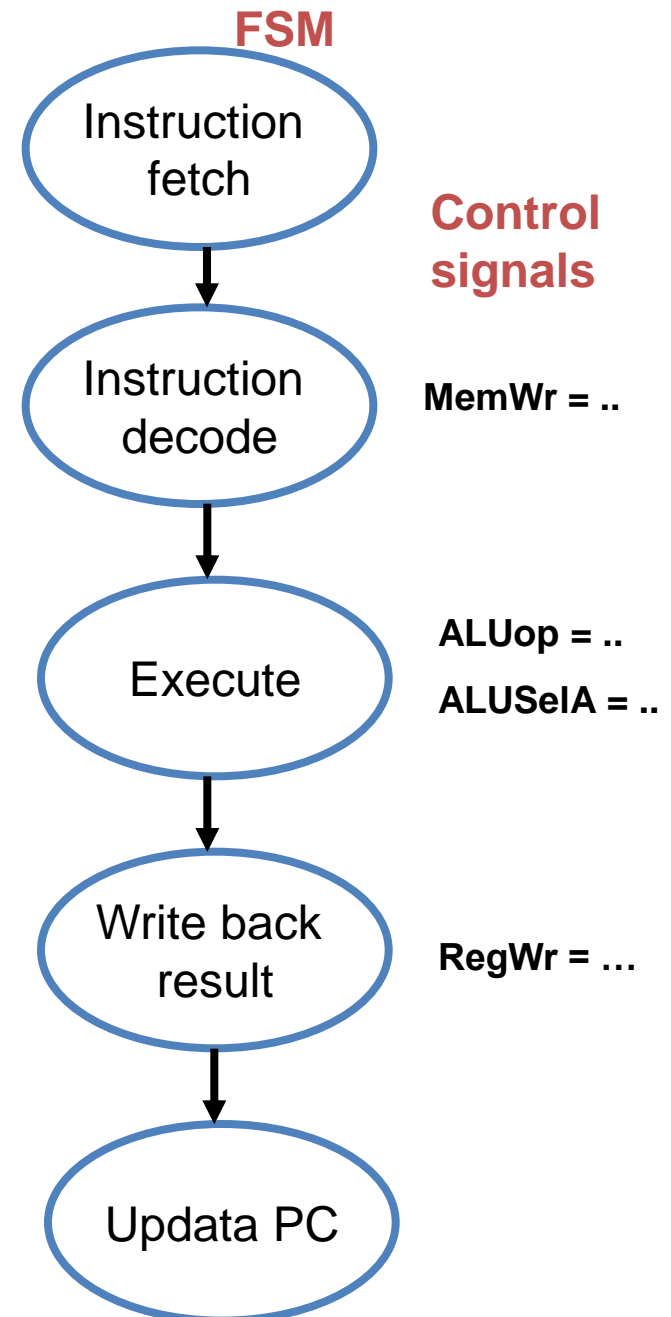
# Steps to execute instructions: R-type


- R-type, e.g. add \$t0, \$t1, \$t2
  - Instruction fetch
  - Instruction decode, read R[rs] and R[rt]
  - Execute instruction: R[rs] op R[rt]
  - Write result back to register R[rd]
  - Update PC:  $PC = PC + 4$
- Can we design a finite state machine to represent these states? And generate different control signals at different states to control the operation of the datapath?
- E.g. design a FSM with 5 states: IF, ID, EX, WB, PC. Each state outputs appropriate control signals to control the datapath to finish adequate operation in a certain state.



# Steps involved in instructions:

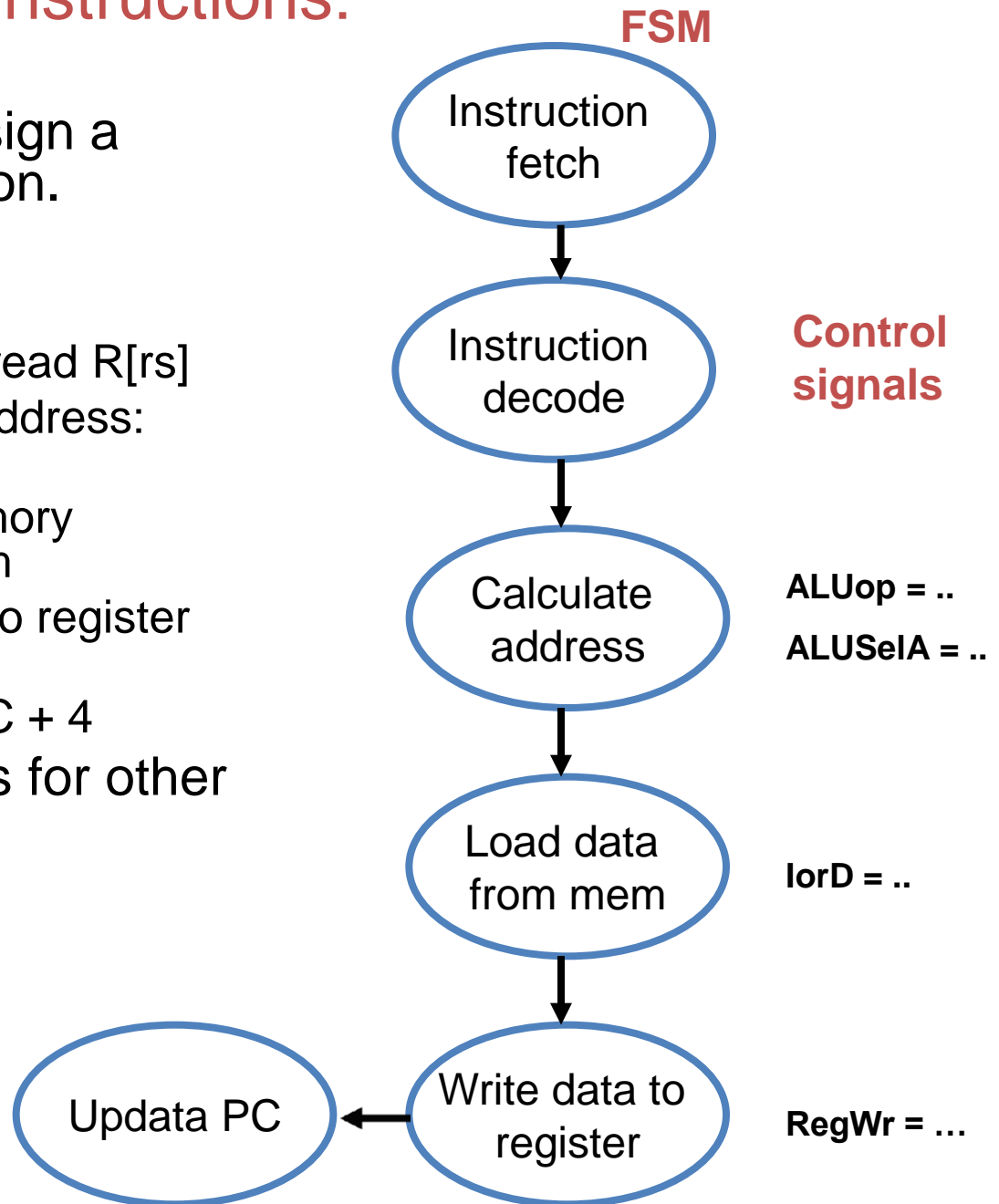
## LW

- Similarly, we can design a FSM for LW instruction.
- Load word
  - Instruction fetch
  - Instruction decode: read  $R[rs]$
  - Calculate memory address:  $R[rs] + Imm$
  - Load data from memory address:  $R[rs] + Imm$
  - Write memory data to register  $R[rt]$
  - Update PC:  $PC = PC + 4$
- We can design FSMs for other instructions.



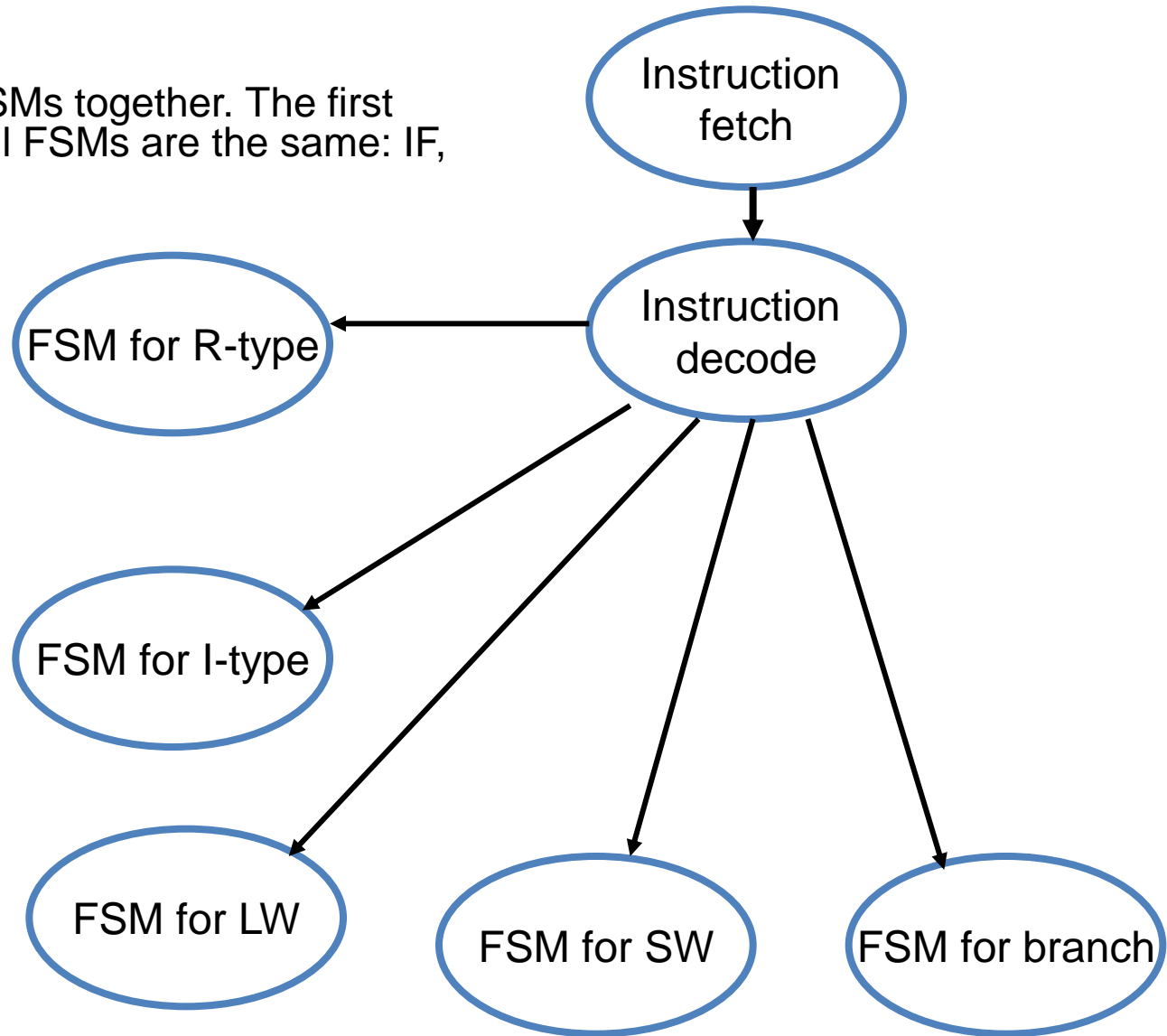
# Control FSM for the multi-cycle processor

- Combine all FSMs together. The first two states of all FSMs are the same: IF, ID.


 
# Design of FSM

- Combinational logic: implement state transition function
  - Can be implemented using “process” statement.
- Sequential logic: change state every clock cycle.
- Output depends on input and pr\_state -> Mealy
- Output depends on pr\_state only -> Moore
- pr\_state: present state
- nx\_state: next state



# Design the sequential part

```
PROCESS
```

```
Begin
```

```
    IF (reset = '1') THEN
```

```
        pr_state <= initial_state;
```

```
    ELSIF (Clk'EVENT AND Clk='1') THEN
```

```
        pr_state <= nx_state;
```

```
    END IF;
```

```
END PROCESS;
```



# Design the combinational part

```
PROCESS (input, pr_state)
Begin
    CASE pr_state IS
        WHEN state0 =>
            IF (input = "01") THEN
                output <= '111';
                nx_state <= state1;
            ELSIF ...
            END IF;
        WHEN state1 =>
            IF (input = "10") THEN
                output <= '001';
                nx_state <= state2;
            ELSIF ...
            END IF;
        ...
    END CASE;
    statenum <= pr_state;

END PROCESS;
```


← Mealy

# Design the combinational part

```
PROCESS (input, pr_state)
Begin
    CASE pr_state IS
        WHEN state0 =>
            output <= '111';           ← Moore
            IF (input = "01") THEN
                nx_state <= state1;
            ELSIF ...
            END IF;
        WHEN state1 =>
            output <= '001';
            IF (input = "10") THEN
                nx_state <= state2;
            ELSIF ...
            END IF;
        ...
    END CASE;
END PROCESS;
```


# Example

State transition diagram:

 

↑  
FSM

The FSM

 

# Entity

```
ENTITY simple_fsm IS
PORT (
    a, b, d, Clk, reset: IN std_logic;
    x: OUT std_logic);
END simple_fsm;
```

# Architecture

```
ARCHITECTURE simple_fsm_ar OF simple_fsm IS
```

```
    signal pr_state: std_logic_vector(1 downto 0);
```

```
    signal nx_state: std_logic_vector(1 downto 0);
```

```
BEGIN
```

```
    combinational part
```

```
    sequential part
```

```
END simple_fsm_ar;
```

# Sequential part

```
PROCESS (reset, Clk)
BEGIN
    IF (reset = '1') THEN
        pr_state <= "00";
    ELSIF (Clk'EVENT AND Clk='1') THEN
        pr_state <= nx_state;
    END IF;
END PROCESS;
```

# Combinational part

```
PROCESS (a, b, d, pr_state)
BEGIN
    CASE pr_state IS
        WHEN "00" =>
            x <= a;
            IF (d = '1') THEN
                nx_state <= "01";
            ELSE
                nx_state <= "00";
            END IF;
        WHEN "01" =>
            x <= b;
            IF (d = '1') THEN
                nx_state <= "00";
            ELSE
                nx_state <= "01";
            END IF;
        WHEN others =>
            NULL;      --No action here
    END CASE;
END PROCESS;
```