

CO102

Computer Hardware

Experiment

Lecture 04: VHDL – Combinational Statement

Liang Yanyan

澳門科技大學
Macau of University of Science and Technology

Combinational Circuits

- Circuits whose outputs depend only on current input values.
 - No storage of past input values.
 - No state.
- Can be analyzed using laws of logic
 - Boolean algebra
 - E.g. $a = b \text{ and } c + d$
- Signals change values immediately according to the assignments.

Concurrent code

- VHDL code is inherently concurrent (parallel).
 - Except that statements inside a PROCESS is sequential (will be addressed later).

entity circuit is

```
    port (x, y : in std_logic;  
          f1 : out std_logic;  
          f2 : out std_logic);
```

end circuit;

architecture boolean_eqn of circuit is

begin

```
    f1 <= x or y;  
    f2 <= x and y;
```

end boolean_eqn;

when/else statement

entity circuit is

```
    port (in1 : in std_logic_vector(1 downto 0);  
          out1 : out std_logic_vector(2 downto 0));
```

end circuit;

architecture curcuit_arch of circuit is

begin

```
    out1 <= "000" when (in1 = "00") else  
            "010" when (in1 = "01") else  
            "011" when (in1 = "10") else  
            "100";
```

end curcuit_arch;

With/select/when statement

entity mux is

```
port ( a, b, c, d : in std_logic;  
      sel : in std_logic_vector(1 downto 0);  
      y: out std_logic);
```

end mux;

architecture mux_arch of mux is

begin

```
    with sel select
```


```
    y <= a when "00",
```

```
        b when "01",
```

```
        c when "10",
```

```
        d when others;
```

```
end mux_arch;
```

 

-- notice “,” instead of “;”

-- cannot use “d when “11””

Tri-state buffer

entity tri_state is

```
    port (ena : in std_logic;
```

```
          input: in std_logic_vector (7 downto 0);
```

```
          output: out std_logic_vector (7 down to 0));
```

```
end tri_state;
```


architecture tri_state_arch of tri_state is

```
begin
```

```
    output <= input when (ena = '0') else
```

```
        (others => 'Z');
```

```
end tri_state_arch;
```

 

'Z' : High Impedance, put 'Z' in all 8 bits of output

Common mistakes

entity circuit is

```
    port (x, y : in std_logic;  
          f : out std_logic);
```

end circuit;

architecture circuit_arch of circuit is

begin

```
    f <= x - y;
```

```
    f <= x + y;
```

end circuit_arch;

Common mistakes

entity circuit is

```
    port (x, y : in std_logic;  
          f, g : out std_logic);
```

end circuit;

architecture circuit_arch of circuit is

begin

```
    f <= x - y;
```

```
    f <= g + y;
```

end circuit_arch;