

CO102

Computer Hardware

Experiment

Lecture 01: Introduction

Liang Yanyan

澳門科技大學

Macau of University of Science and Technology

General References

- Instructor: Dr. Liang Yanyan (梁延研)
 - Email: yyliang@must.edu.mo
 - Tel: 88971997
 - Office: A218
- Grading Information
 - Grade determinates
 - Labs 50%
 - Final Exam 50%
- Please submit your lab reports to Moodle.

General References

- www.vhdl.org
- www.fpga.com.cn
- www.opencore.com
-
- Some Resource in FTP
 - Username: yyliang_stu
 - Password: ^%+q2Hkn
 - Link: <ftp://ftp.must.edu.mo/>
- Textbook:
 - VHDL Design Representation and Synthesis, Armstrong and Gray, Prentice Hall.
 - Digital Design: An Embedded Systems Approach Using VHDL, Peter J. Ashenden, Morgan Kaufmann.

Outline

Index	Topic	Hours	Teaching Method
1	Introduction to ASIC design and programmable logic device.	4	Lecture
2	Introduction to VHDL.	2	Lecture
	Lab 1. Implementation of Basic operation of ALU using ISE Design Suite.	2	Lab
3	Using Port Map.	2	Lecture
	Lab 2. Building Full-adder Using Port Map.	2	Lab
4	Combinational Statement.	2	Lecture
	Lab 3. Digital Display and Gray Codes.	2	Lab
5	Sequential Statement.	2	Lecture
	Lab 4. Accumulator; Multiplier Using Booth Algorithm.	2	Lab
6	Lab 5. 12-hour Clock.	4	Lab
7	Finite State Machine.	2	Lecture
	Lab 6. Random number generator and Multi-cycle Processor Control.	2	Lab
8	Lab 7. Register file and memory.	4	Lab
9-10	Lab 8. Single Cycle Processor.	8	Lab
11	Lab 9. FFT Implementation.	4	Lab
12-14	Lab 10. Single Cycle Processor.	12	Lab
15	Summary and Exam.	4	Lecture

Computer Design

Instruction Set Design

- Machine Language
 - Compiler View
 - "Computer Architecture"
 - "Instruction Set Processor"
- "Building Architect"

Computer Hardware Design

- Machine Implementation
 - Logic Designer's View
 - "Processor Architecture"
 - "Computer Organization"
- "Construction Engineer"


Few people design computers! Very few design instruction sets!

Many people design computer components.

Very many people are concerned with computer function, in detail.


The Big Picture

 - What is inside a computer?
- How does it execute my program?




The Big Picture

 
- The Five Classic Components of a Computer



Computer Organization

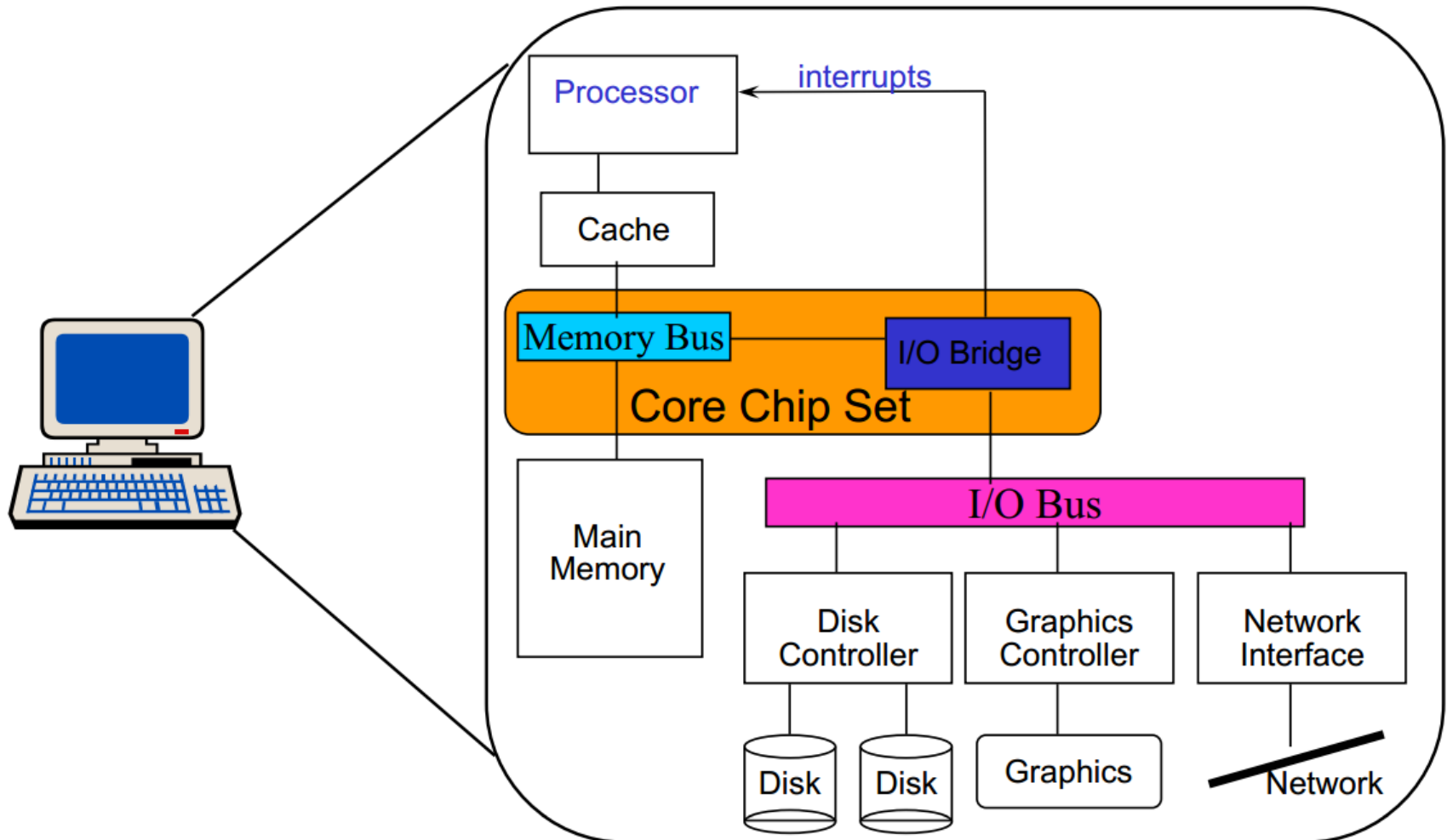


Computer Organization

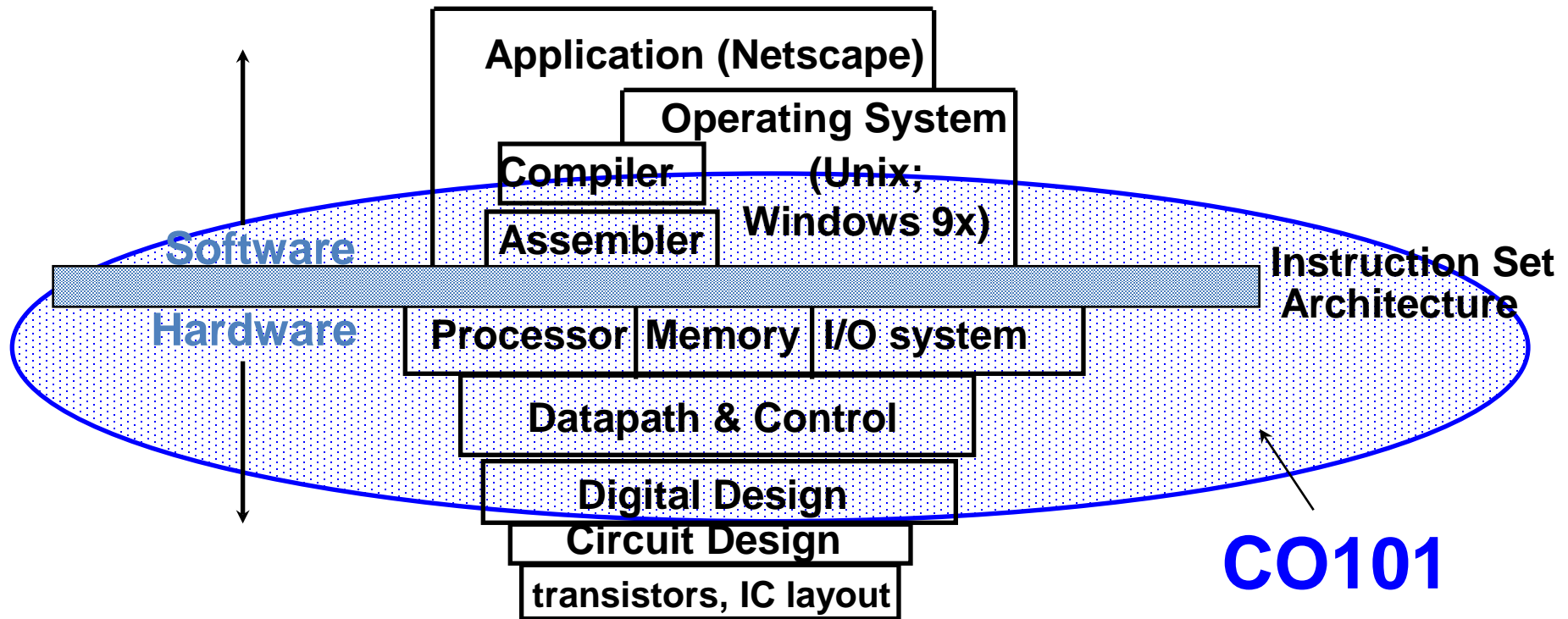

- Key Idea: levels of abstraction

The Evolution of Computer Hardware

 - When was the first transistor invented?




1947 - the bi-polar transistor – by Bardeen *et.al* at Bell Laboratories

UNIVAC I (Universal Automatic Computer) – the first commercial computer in USA



The Evolution of Computer Hardware

 - When was the first IC (integrated circuit) invented?




1958, by Jack Kilby@Texas Instruments, by hand, several transistors, resistors and capacitors on a single substrate.

IBM System/360, 2MHz,
128KB ~ 256KB




The Evolution of Computer Hardware

- When was the first Microprocessor?

 


1971, Intel 4004

 

The History of Intel
Processors:

<https://www.youtube.com/watch?v=Qu2njWY3Hjk>

The Chip Manufacturing Process

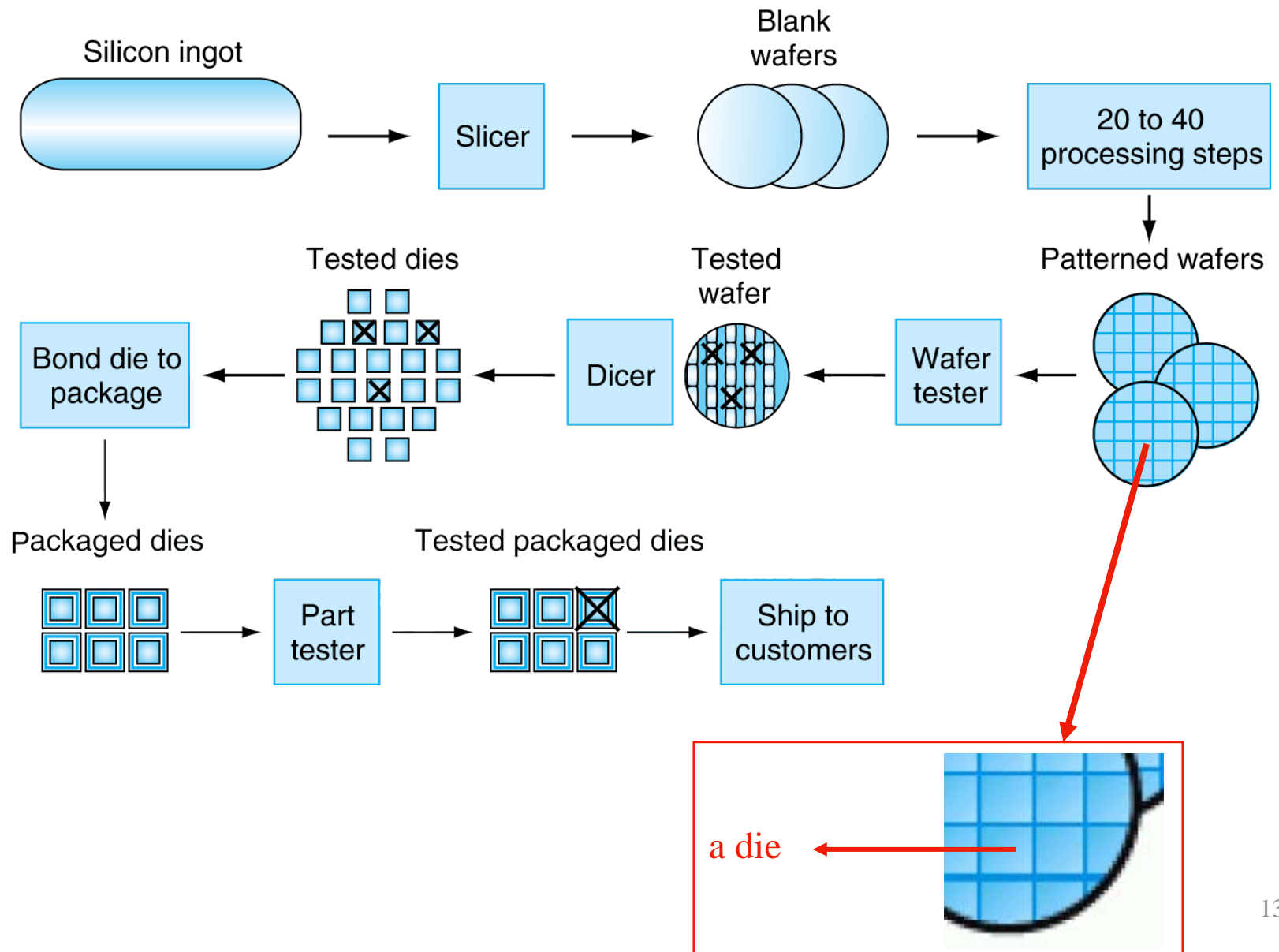


Analog vs. Digital

- Analog Signal

- Vary in a smooth way over time.
- Analog data are continuous valued
 - Example: audio, video


- Digital Signal

 - Maintains a constant level then changes to another constant level (generally operate in one of the two states).
- Digital data are discrete value.
 - Example: computer data.




Digital Systems

Digital vs. Analog Waveforms

 


Digital:
only assumes discrete values

 

Analog:
values vary over a broad range continuously

Truth Table

 - A means for describing how a logic circuit's output depends on the logic levels present at the circuit's inputs.
- The number of input combinations will equal 2^N for an N-input truth table.



Inputs		Output
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Digital Hardware Systems

Boolean Algebra and Logical Operators

Algebra: variables, values, operations

In Boolean algebra, the values are the symbols 0 and 1

If a logic statement is false, it has value 0

If a logic statement is true, it has value 1

Operations: AND, OR, NOT

X	Y	X AND Y
0	0	0
0	1	0
1	0	0
1	1	1


X	Y	X OR Y
0	0	0
0	1	1
1	0	1
1	1	1

X	NOT X
0	1
1	0

Case Study of a Simple Logic Design:


Seven Segment Display

- Chip to drive digital display

 


B3	B2	B1	B0	Val
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9


Case Study (cont.)

 


B3	B2	B1	B0	Val	L1	L2	L3	L4	L5	L6	L7
0	0	0	0	0	1	0	1	1	1	1	1
0	0	0	1	1	0	0	0	0	0	1	1
0	0	1	0	2	1	1	1	0	1	1	0
0	0	1	1	3	1	1	1	0	0	1	1
0	1	0	0	4	0	1	0	1	0	1	1
0	1	0	1	5	1	1	1	1	0	0	1
0	1	1	0	6	1	1	1	1	1	0	1
0	1	1	1	7	1	0	0	0	0	1	1
1	0	0	0	8	1	1	1	1	1	1	1
1	0	0	1	9	1	1	1	1	0	1	1

 


How do computers work?

 


The basic unit: repeater

 


Basic logic unit: NOT

 



Basic logic unit: buffer



 


Basic logic unit: AND

 


AND	0	1
0	0	0
1	0	1

  

   



Basic logic unit: OR

 

OR	0	1
0	0	1
1	1	1



Half-adder and Full-adder

  





Basic logic unit: NAND and NOR

AND	0	1
0	0	0
1	0	1

OR	0	1
0	0	1
1	1	1

NAND	0	1
0	1	1
1	1	0


NOR	0	1
0	1	0
1	0	0

    

Case Study


- Implement L4:

B3	B2	B1	B0	L4
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1

 

Some gate level implementation
of the Boolean function for L4


Building a 1-bit Binary Half Adder

 


Inputs		Outputs	
A	B	C	S
0	0	0	0
1	0	0	1
0	1	0	1
1	1	1	0

- A: input
- B: input
- S: output
- C: output

- Using two half adders to

 

Building a 1-bit Binary Full Adder

 

A	B	carry_in	carry_out	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$S = A \text{ xor } B \text{ xor } \text{carry_in}$$
$$\text{carry_out} = A \& B \mid A \& \text{carry_in} \mid B \& \text{carry_in}$$

(majority function)

How can we use it to build a 32-bit adder?

How can we modify it easily to build an adder/subtractor?


Building 32-bit Adder

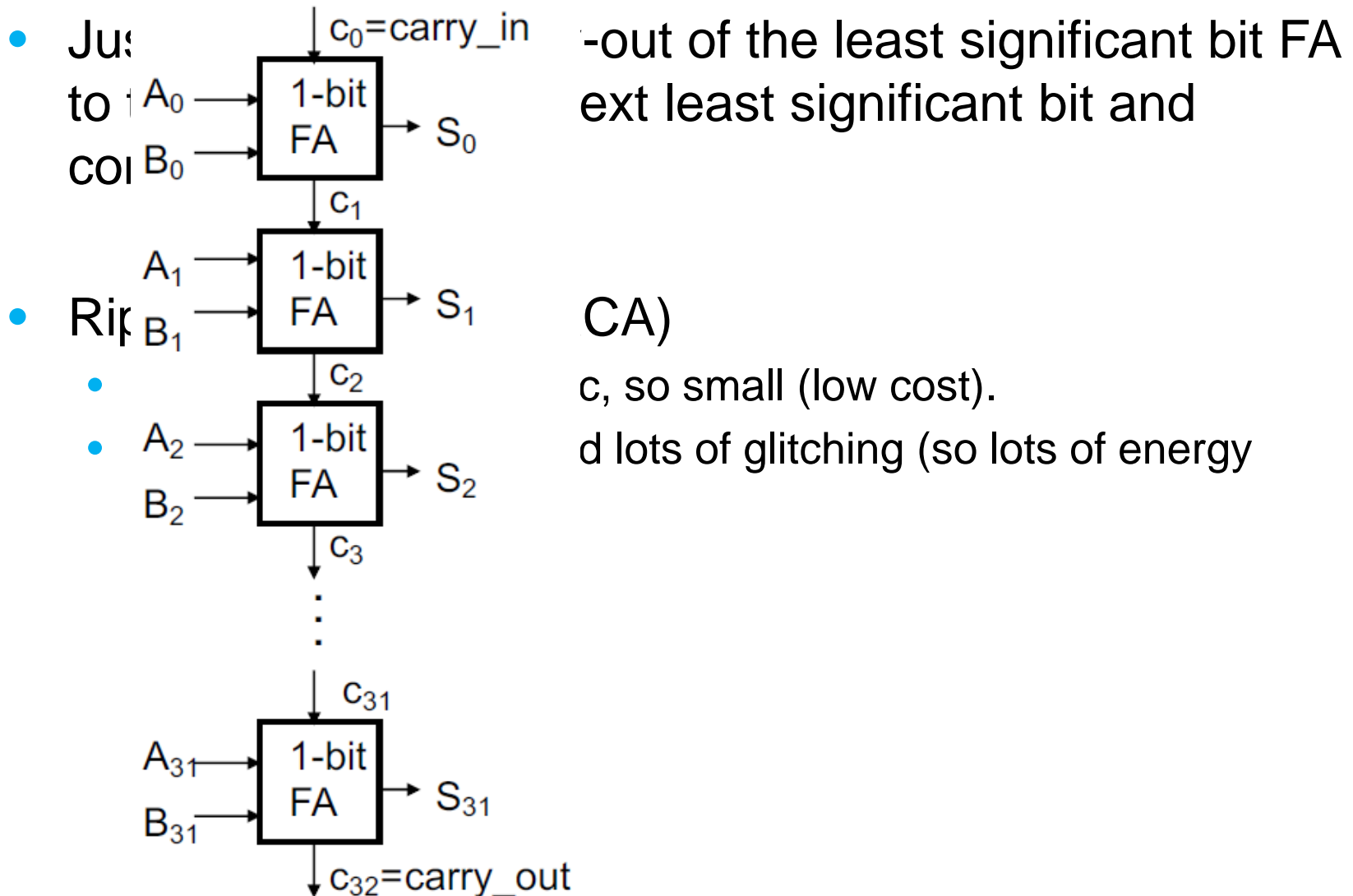


Gate Representations of a Digital Design

most widely used primitive building block in digital system design

Standard Logic Gate Representation

 

Half Adder Schematic

 


Net: electrically connected collection of wires

Netlist: tabulation of gate inputs & outputs
and the nets they are connected to

Representations of a Digital Design: Gates

Full Adder Schematic

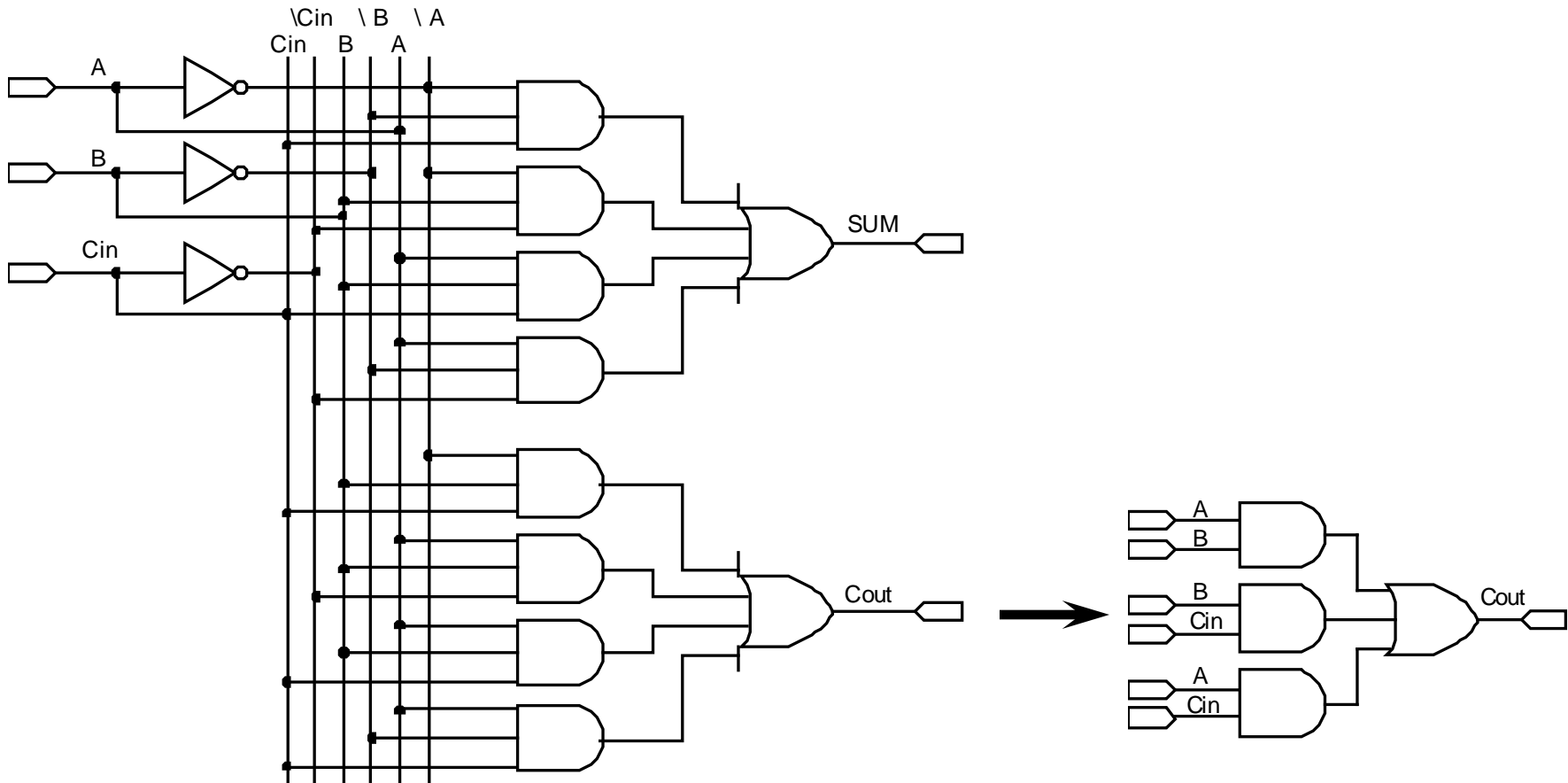

Fan-in: number of inputs to a gate

Fan-out: number of gate inputs an output is connected to

Technology "Rules of Composition" place limits on fan-in/fan-out


Block Representation of a Digital Design

structural organization of the design


black boxes with input and output connections

corresponds to well defined functions

 concentrates on how the components are composed by wiring



 
Full Adder realized in terms of composition of half adder blocks



Block diagram representation of the Full Adder

Waveform Representation

 dynamic behavior of a circuit
real circuits have non-zero delays












Output changes are delayed from input changes

The propagation delay is sensitive to paths in the circuit




Outputs may temporarily change from the correct value to the wrong value back again to the correct value: this is called a *glitch* or *hazard*

Feedback and Flip-Flops

     

   
 


Inputs		Outputs	
S	R	Q	\bar{Q}
1	0	1	0
0	1	0	1
0	0	Q	\bar{Q}
1	1	Disallowd	

   

Inputs		Outputs
Data	Hold That Bit	Q
0	1	0
1	1	1
0	0	Q
1	0	Q



Inputs		Outputs	
D	Clk	Q	Q-bar
0	1	0	1
1	1	1	0
X	0	Q	Q-bar

  



An edge-triggered D-type flip-flop

- The idea here is that the Clock input controls both the first stage and the second stage. But notice that the clock is inverted in the first stage. This means that the first stage works exactly like a D-type flip-flop except that the Data input is stored when the Clock is 0. The outputs

Inputs		Outputs	
D	clk	Q	\bar{Q}
1	0	0	1
1	↑	1	0
0	1	1	0
0	0	1	0
0	↑	0	1
1	1	0	1

  

An edge-triggered D-type flip-flop

  


Registers



- A register is a group of flip-flops.
- An n-bit register is made of n flip-flops and can store n bits.
- A register may have additional combinational gates to perform certain operations.


4-Bit Register

 - A simple 4-bit register can be made with 4 D flip-flops.
- They have a Common Clock.
 - At each positive-edge, 4 bits are loaded in parallel.
 - Previous data is overwritten.
- Common Clear
 - Asynchronous clear
 - When clear = 0, all flip-flops are cleared. i.e



4-bit Shift Register


- Serial-in and Serial-out (SISO)

 




- A simple 4-bit shift register can be made with 4 D-type flip-flops.
- They have a Common Clock.
 - At each positive-edge, 1 bit is shifted in
 - Rightmost bit is discarded
- Which direction is this register shifting?

Multiply Hardware

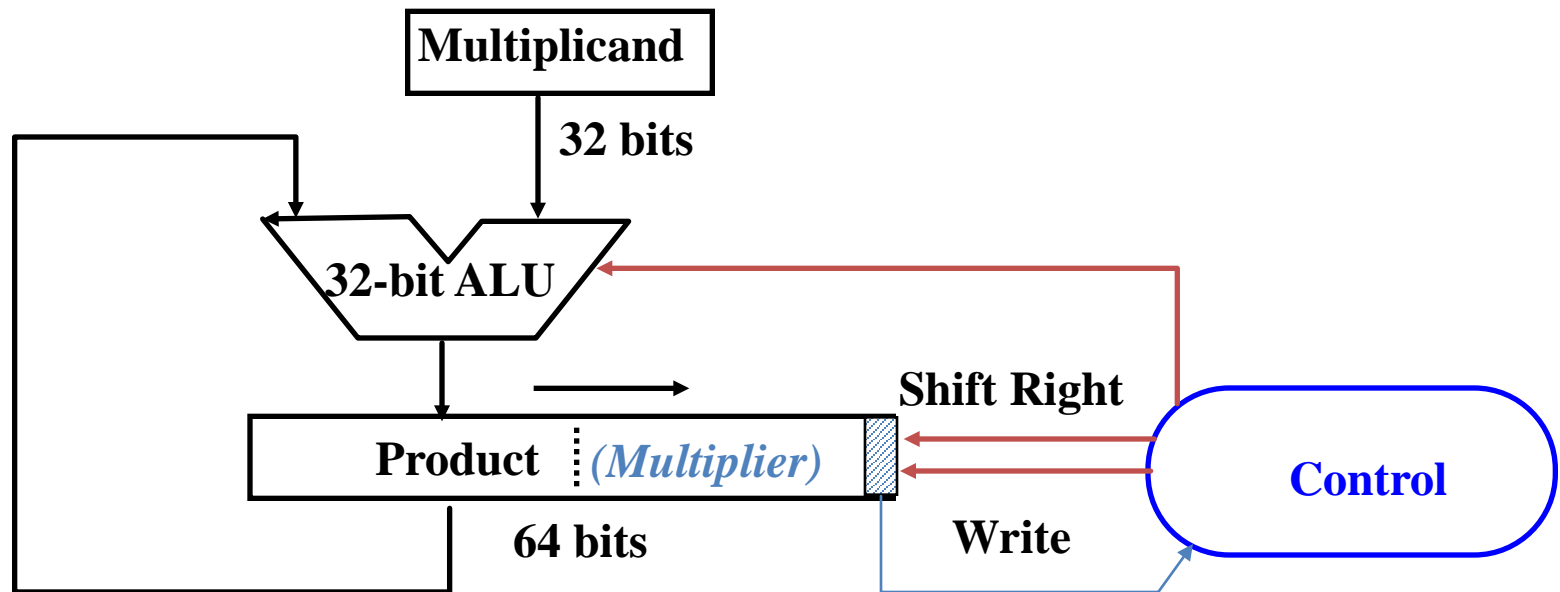- 32-bit Multiplicand register, 32-bit ALU, 64-bit Product register, (Multiplier register is encapsulated in product register).






Frequency Divider

   

Increasing binary numbers

  - At each positive transition of the Clock, some Q outputs might change and some might not, but together they reflect increasing binary numbers.



 


Programmable Logic Devices (PLD)


- A programmable logic device or PLD is an electronic component used to build reconfigurable digital circuits. Unlike a logic gate, which has a fixed function, a PLD has an undefined function at the time of manufacture. Before the PLD can be used in a circuit it must be programmed (i. e. reconfigured).
- ROM: Read Only Memory
- PAL: Programmable Array Logic
- GAL: Generic Array Logic (Derived from PAL, using OLMC—Output Logic Macro Cell)
- EPLD: Erasable Programmable Logic Device
- CPLD: Complex Programmable Logic Device
- FPGA: Field Programmable Gate Array



PLD vs. ASIC

 ASIC: Application Specific Integrated Circuit





GALs and PALs

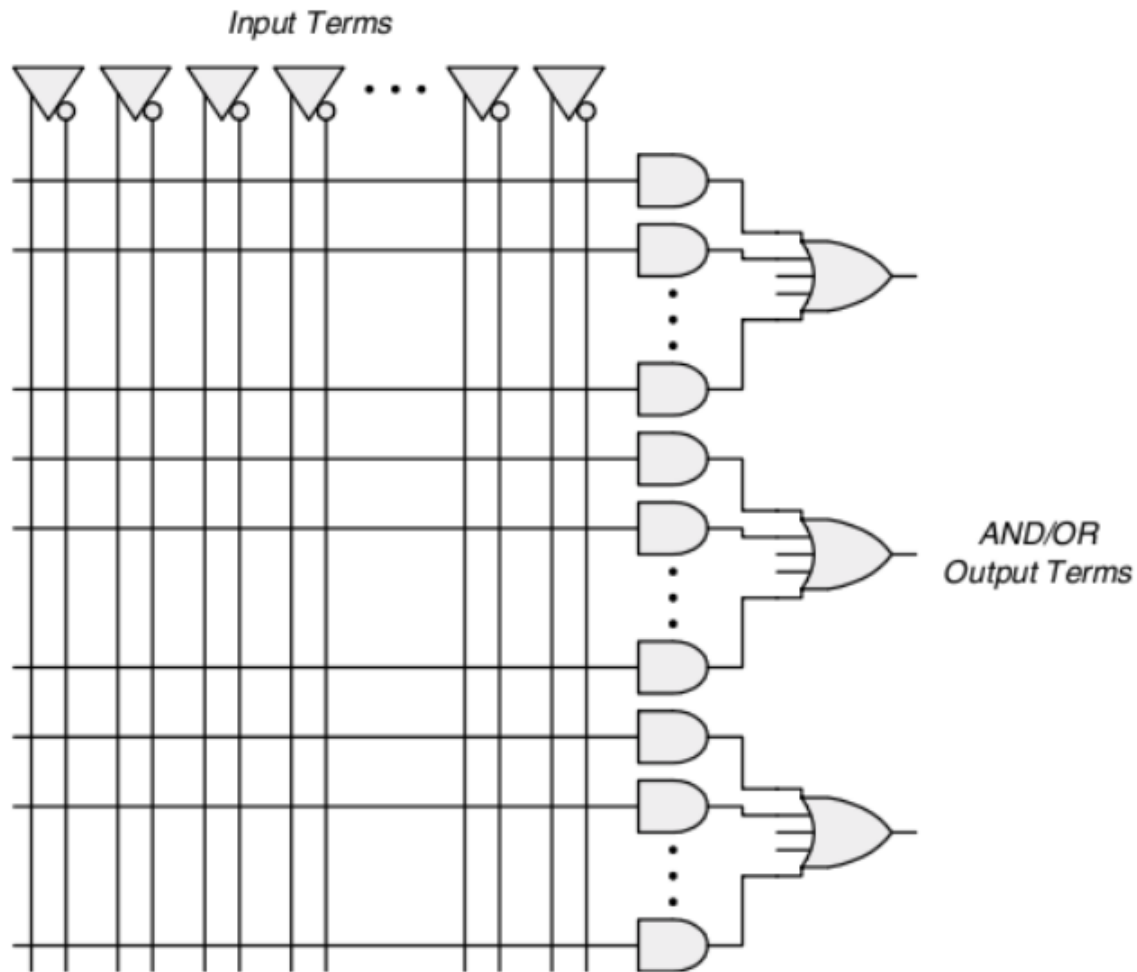

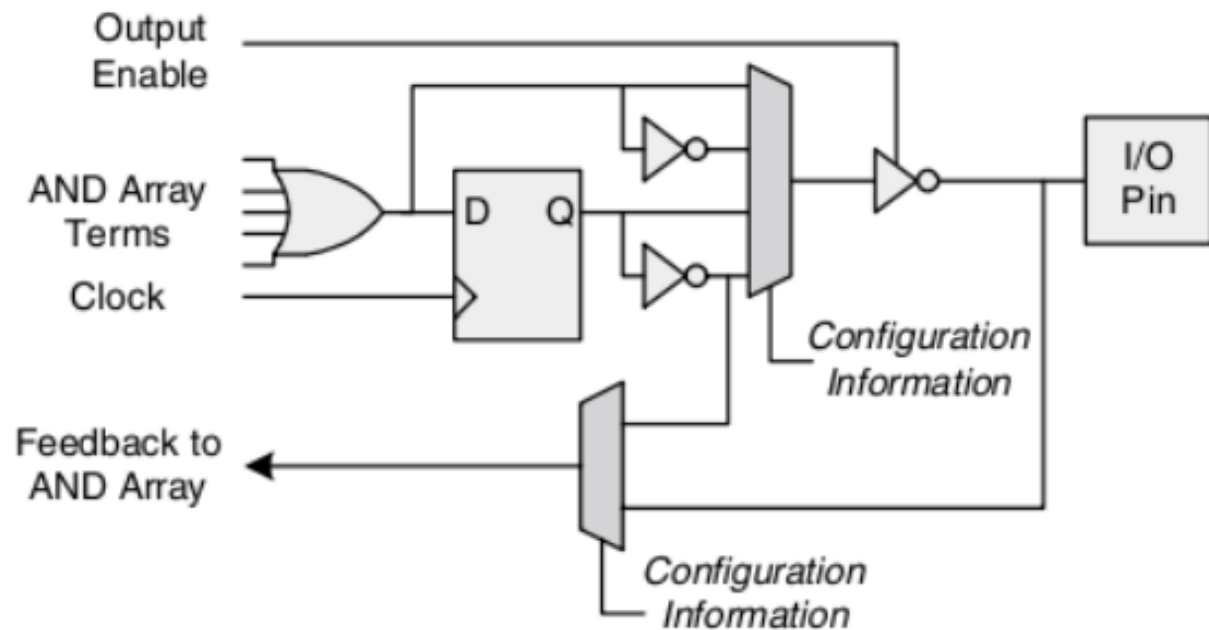 

Using ROMs to Implement a Function

  


Example: Using 16x4 ROM to implement a function

- Implement the following function:

$$F_1(w,x,y,z) = w'x'yz + w'xyz' + w'xyz + wx'y'z' + wx'yz' + wxyz'$$

$$F_2(w,x,y,z) = w'x'y'z' + w'x$$

 

Example: Using 4x4 PAL to implement a function

Implement the following function:

$$F_1(w,x,y,z) = w'x'yz + wx'yz'$$

$$F_2(w,x,y,z) = w'x'yz + wx'yz' + w'xy'z' + wxyz$$


$$F_3(w,x,y,z) = w'x'y'z' + w'x'y'z + w'x'yz' + w'x'yz$$

First we can reduce the terms like as follows:

$$\begin{aligned} F_2(w,x,y,z) &= w'x'yz + wx'yz' + w'xy'z' + wxyz \\ &= F_1 + w'xy'z' + wxyz \end{aligned}$$


$$\begin{aligned} F_3(w,x,y,z) &= w'x'y'z' + w'x'y'z + w'x'yz' + w'x'yz \\ &= w'x'(y'z' + y'z + yz' + yz) \\ &= w'x' \end{aligned}$$

=>

 


Complex Programmable Logic Device (CPLD)

 - (CPLD) is capable of implementing a circuit with upwards of 10,000 logic gates. Sequential circuits can also be implemented with CPLDs.




Internal Structure of CPLDs

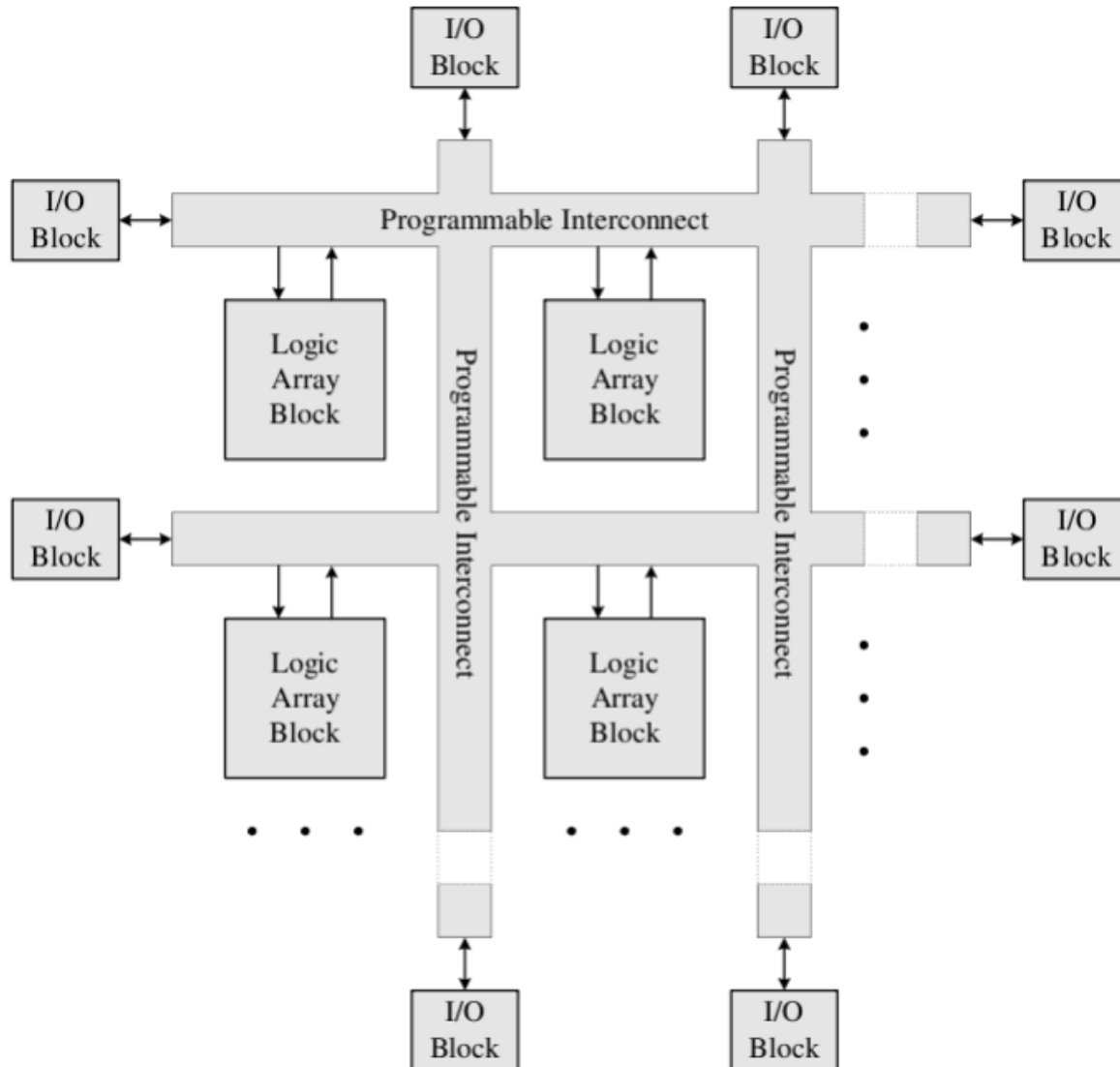


Field Programmable Gate Array (FPGA)

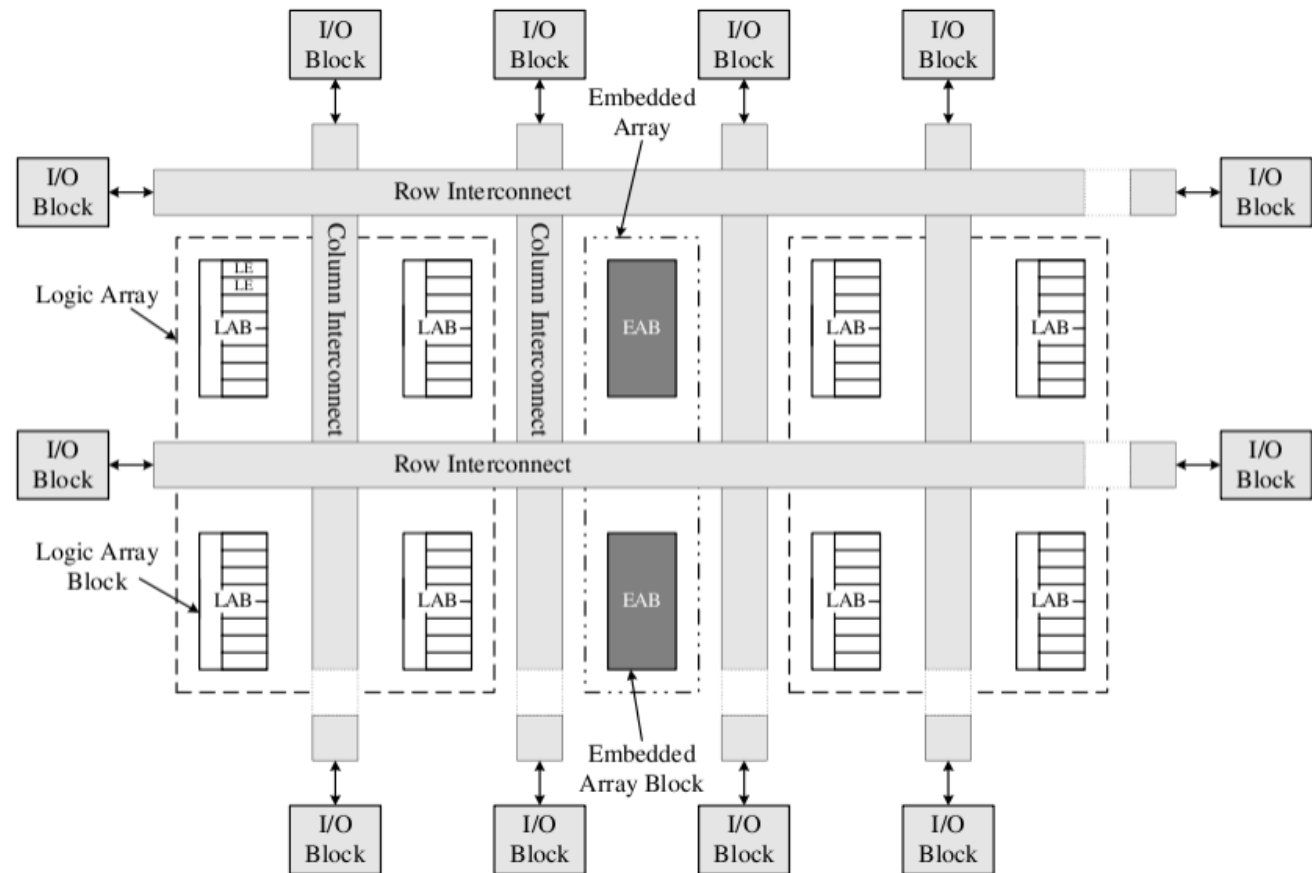- Field programmable gate arrays (FPGAs) are complex programmable devices that can be configured to implement a wide range of digital logic functions, including combinational logic, sequential logic, and memory (RAM bits), as a single chip.



FPGA Internal Structure

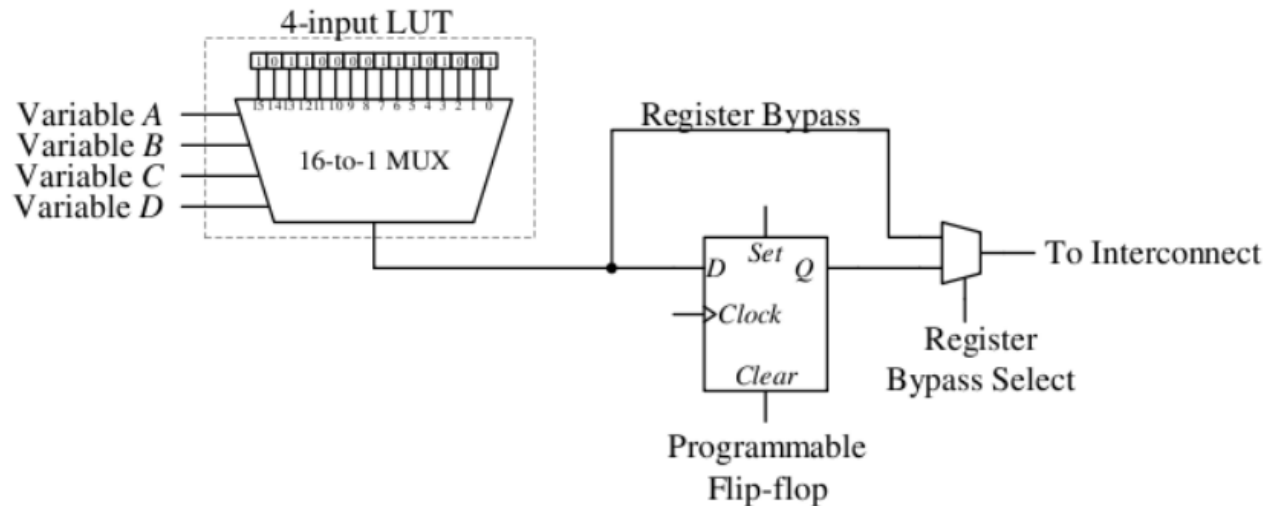


All the EABs, LABs, and I/O elements, are connected together via the FastTrack interconnect, which is a series of fast row and column buses that run the entire length and width of the device. The interconnect contains programmable switches so that the output of any block can be connected to the input of any other block.

Each I/O pin in an I/O element is connected to the end of each row and column of the interconnect and can be used as either an input, output, or bi-directional port.

EDA: Electronic Design Automation

The core of modern electronic design technology has increasingly turned to **electronic design automation** technology based on computer

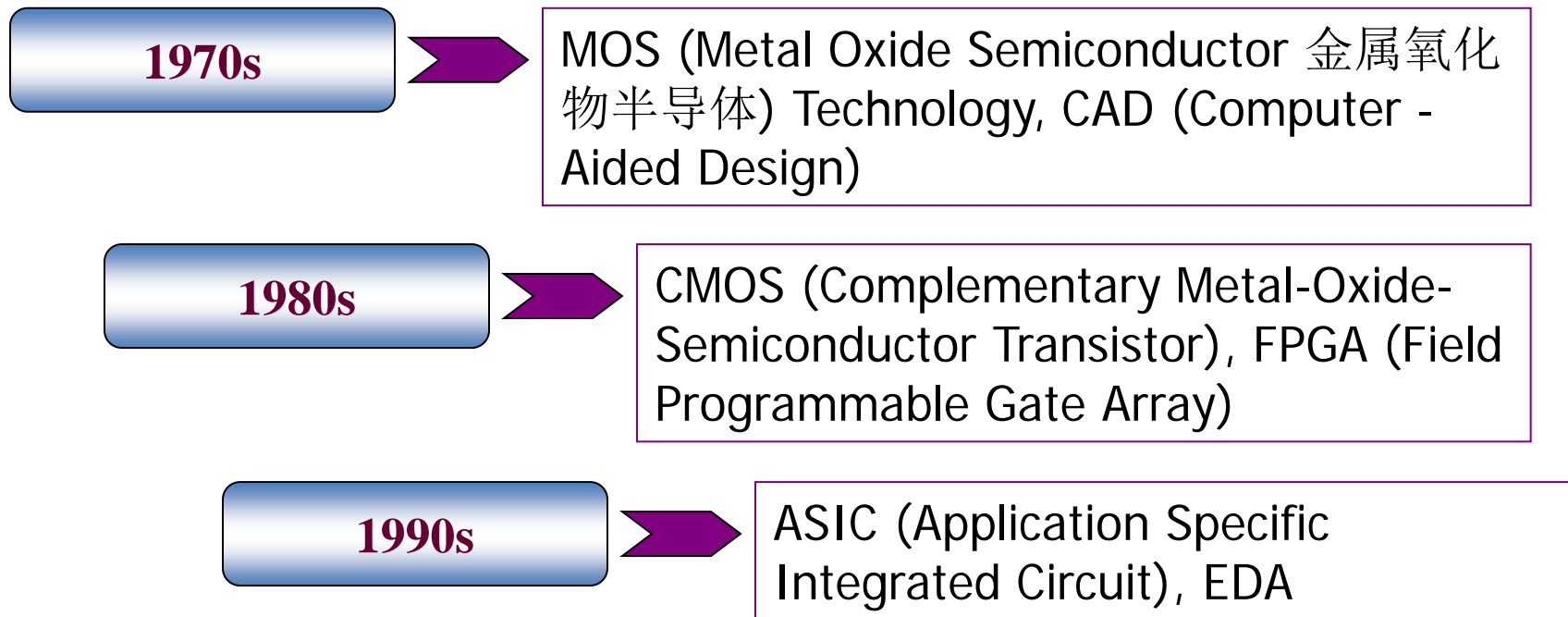Three stages of the development of EDA technology



Programming Language

- Hardware Description Language (HDL)
 - Can we use C or Java as HDL?
- A computer programming language
 - Semantics (“meaning”)
 - Syntax (“grammar”)
- Develop of a language
 - Study the characteristics of the underlying processes.
 - Develop syntactic constructs and their associated semantics to model and express these characteristics.

Traditional PL

- Modeled after a sequential process
 - Operations performed in a sequential order
 - Help human's thinking process to develop an algorithm step by step
 - Resemble the operation of a basic computer model

HDL

- Characteristics of digital hardware
 - Connections of parts
 - Concurrent operations
 - Concept of propagation delay and timing
- Characteristics cannot be captured by traditional PLs
- Require new languages: HDL

Modern HDL

- Capture characteristics of a digital circuit:
 - entity
 - connectivity
 - concurrency
 - timing
- Cover description
 - In Gate level and Register-Transfer level (RTL)
 - In structural view and behavioral view

HDL

HDL

VHDL

Verilog HDL

ABEL

AHDL

SystemVerilog

SystemC


History of VHDL

- VHDL
 - VHSIC (Very High Speed Integrated Circuit)
 - Hardware
 - Description
 - Language
- 1980——VHSIC plan of the US department of defense
- 1985——First Version
- 1987——IEEE Standard 1076 (VHDL'87)
- 1993——IEEE Standard 1076 (VHDL'93)


Why using VHDL?

- A Language For Synthesis
 - Independent to its physical implementation
 - A standard accepted by most EDA (synthesis) software
 - Easy to maintain
 - Code reuse
- A Language For Simulation
 - Supported by most EDA (simulator) tools
 - Help engineers verify their design
 - HW-SW mixed system design


Digital System Design Flowchart (ASIC)

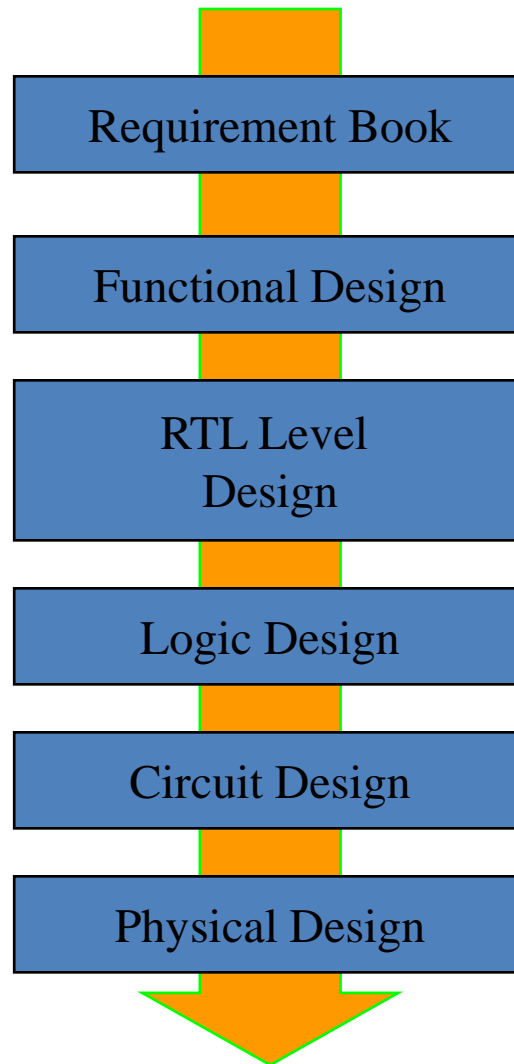

Digital System Design Flowchart (FPGA)


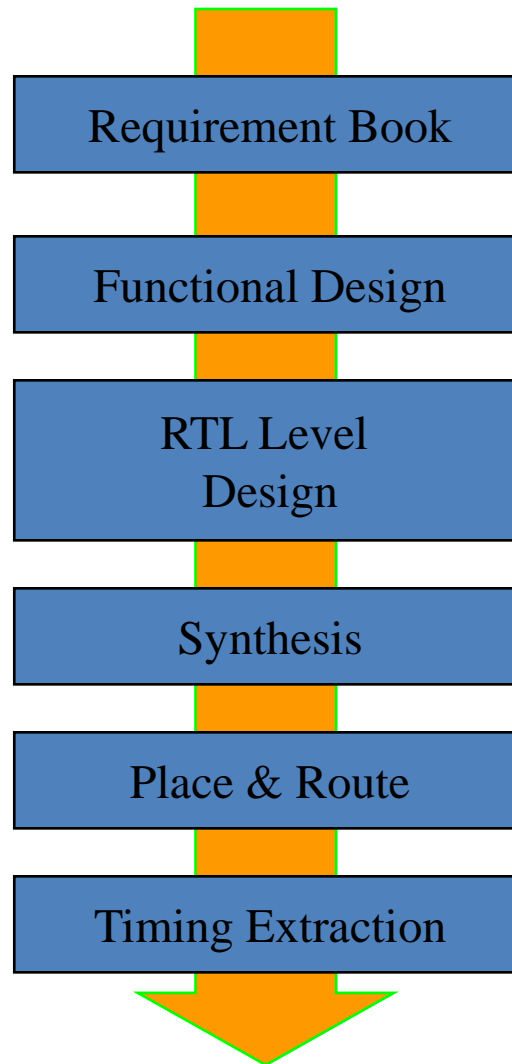


Flowchart Example (1)


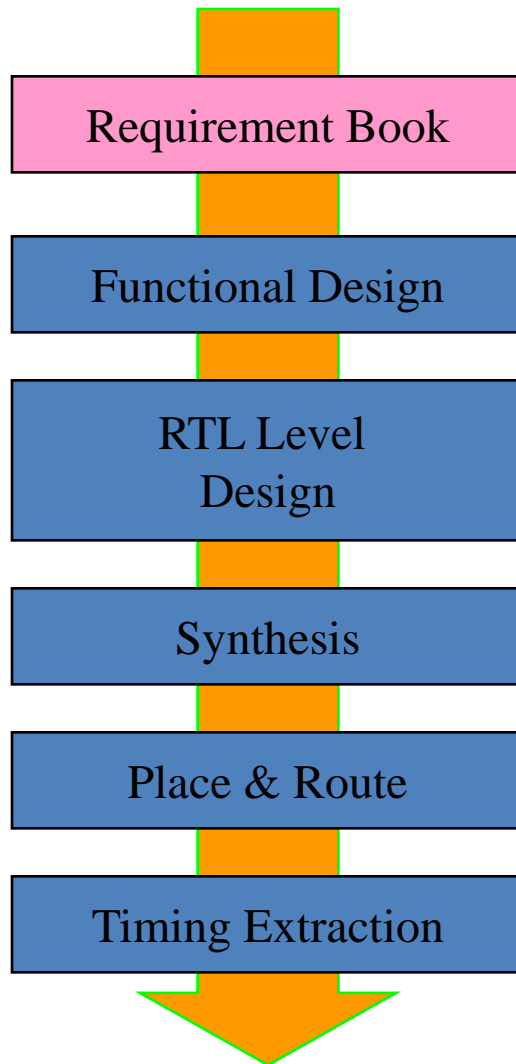


- 电子钟
- 定时闹铃
- 手动调时
- 定时误差微调



Flowchart Example (2)

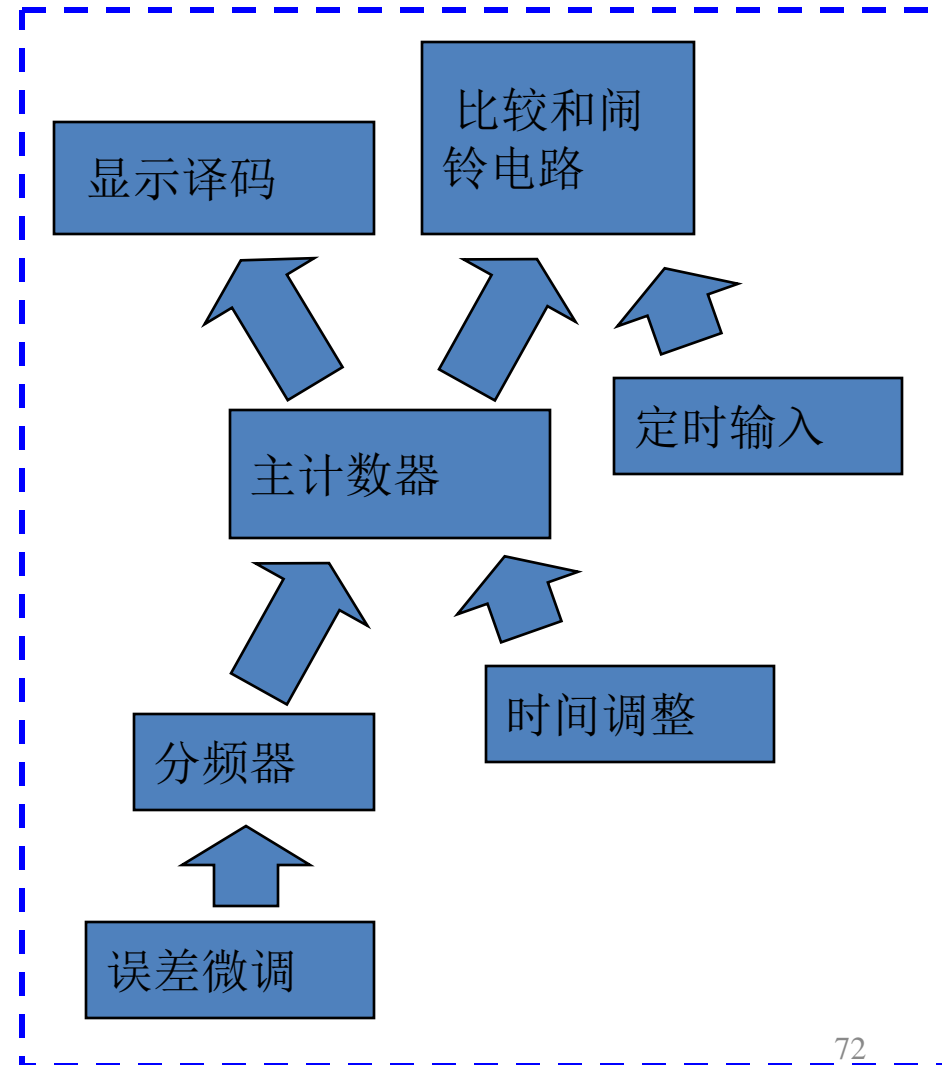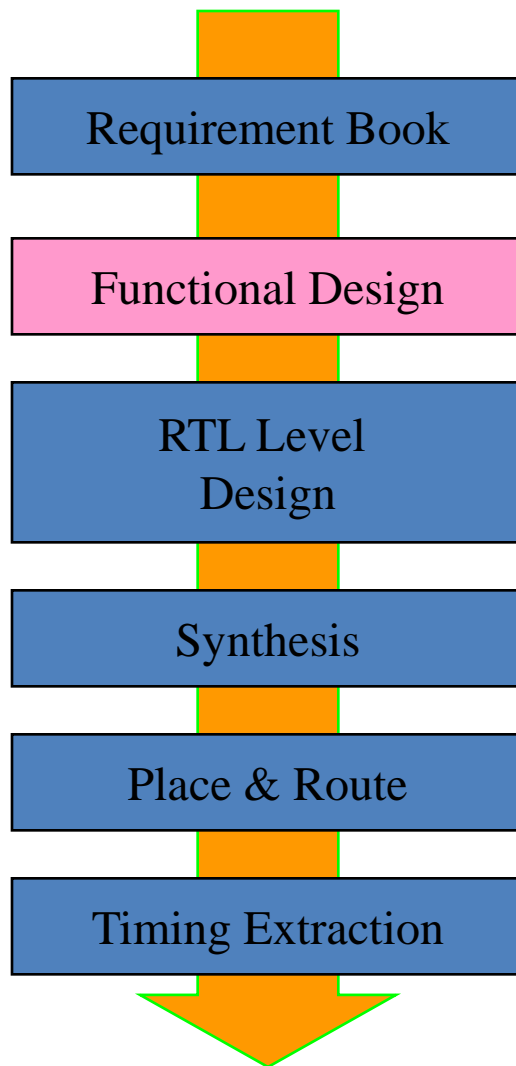



Flowchart Example (3)

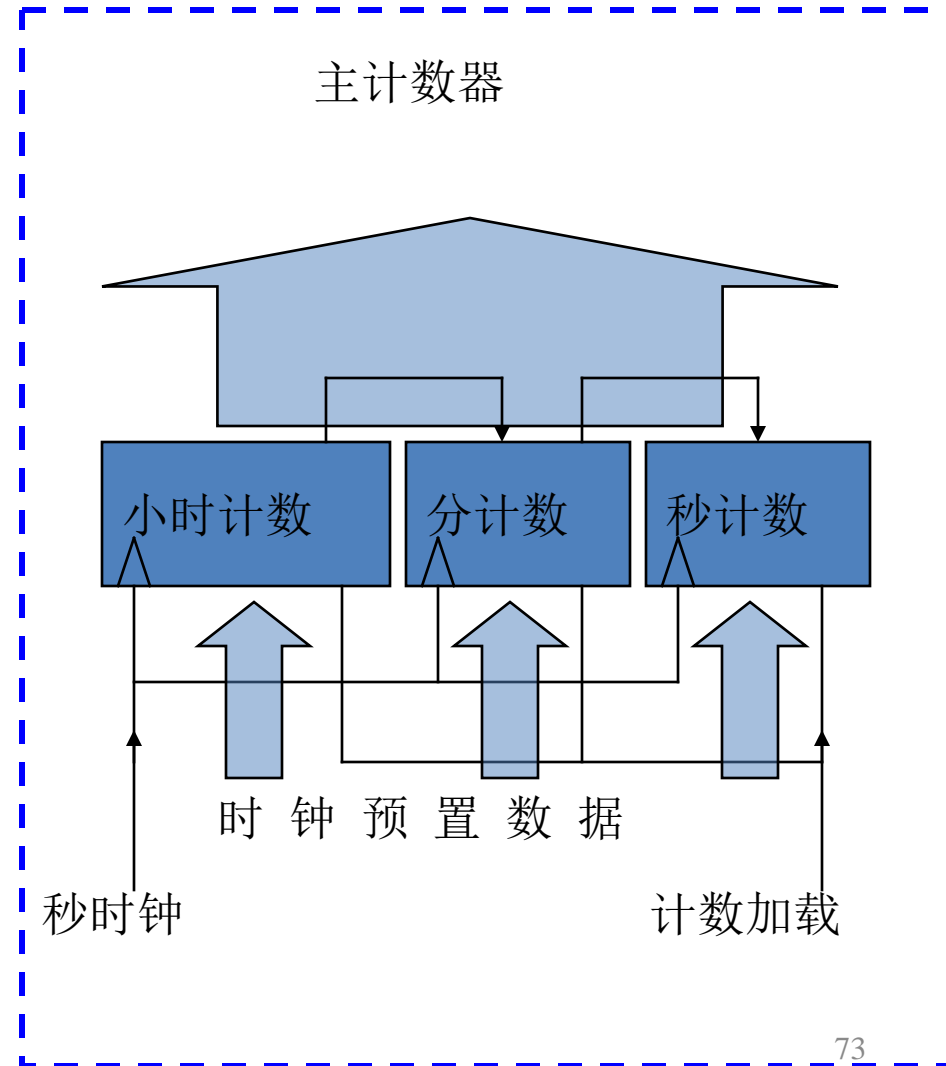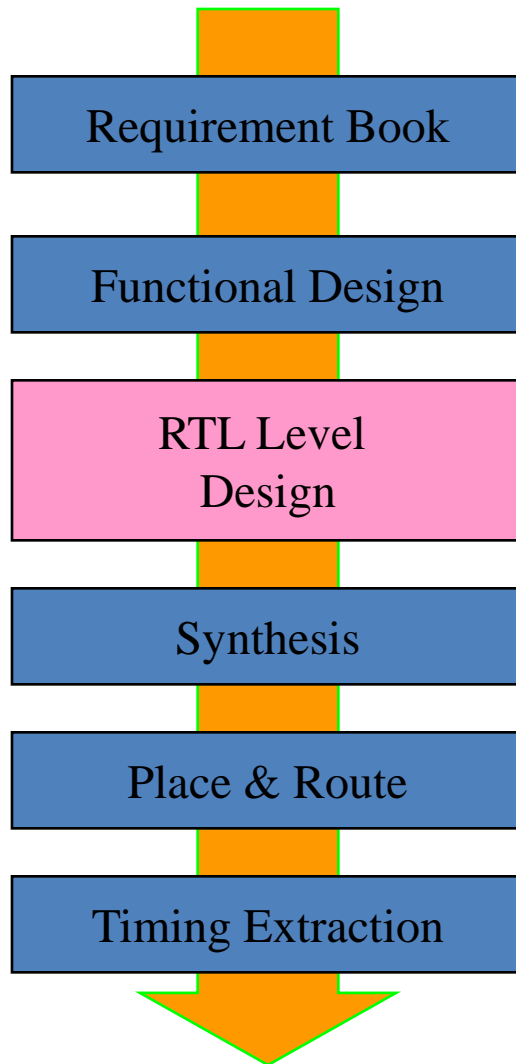


Flowchart Example (4)

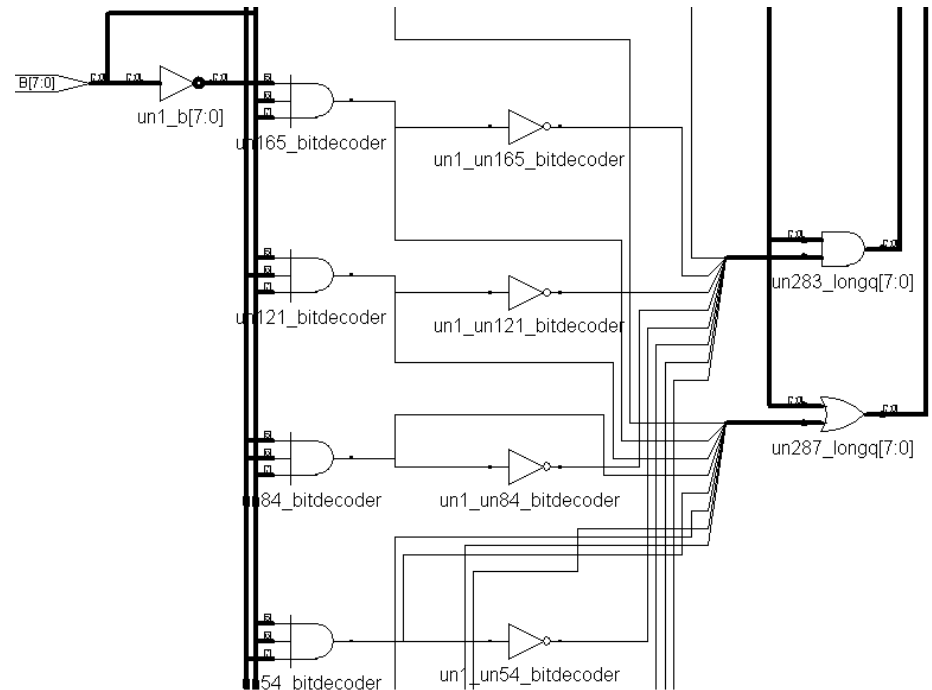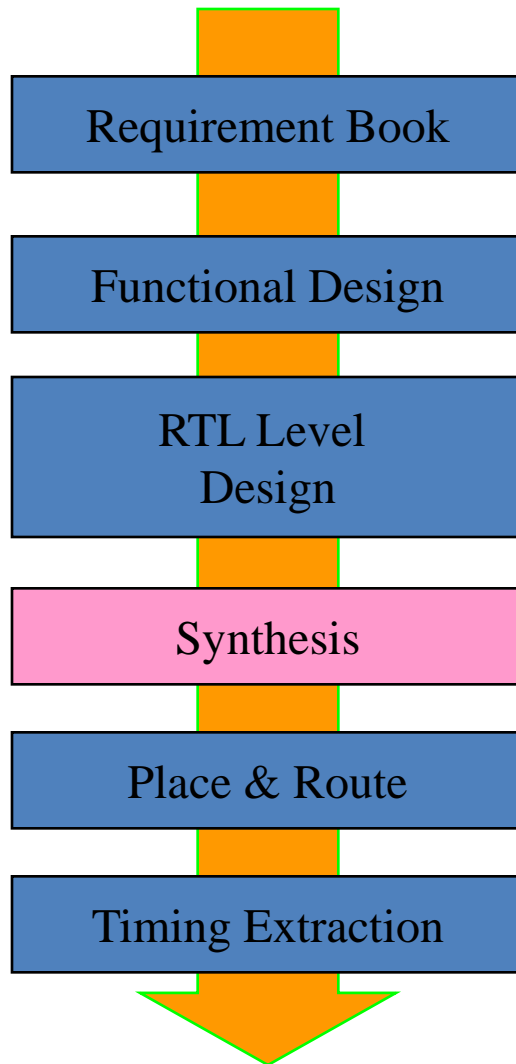

Flowchart Example (5)

 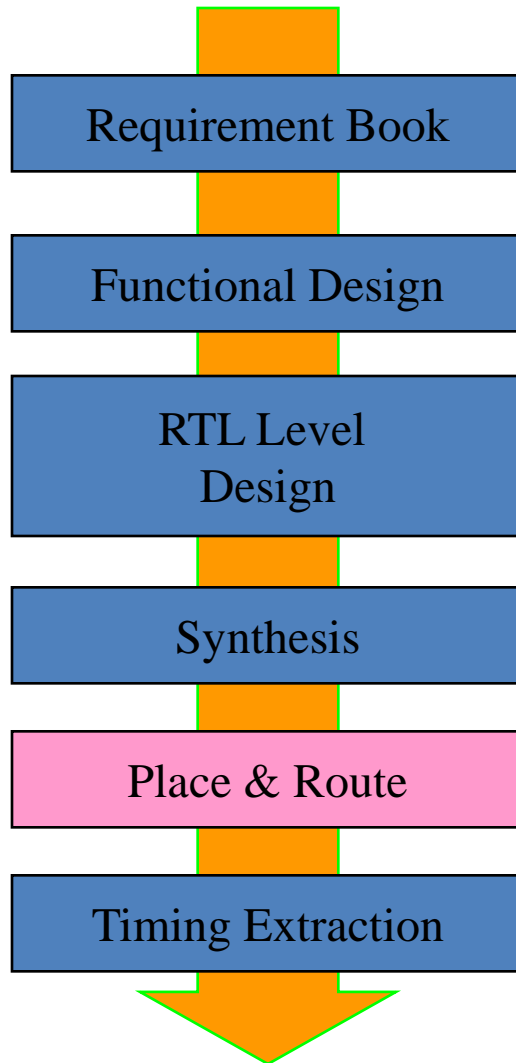


Flowchart Example (6)

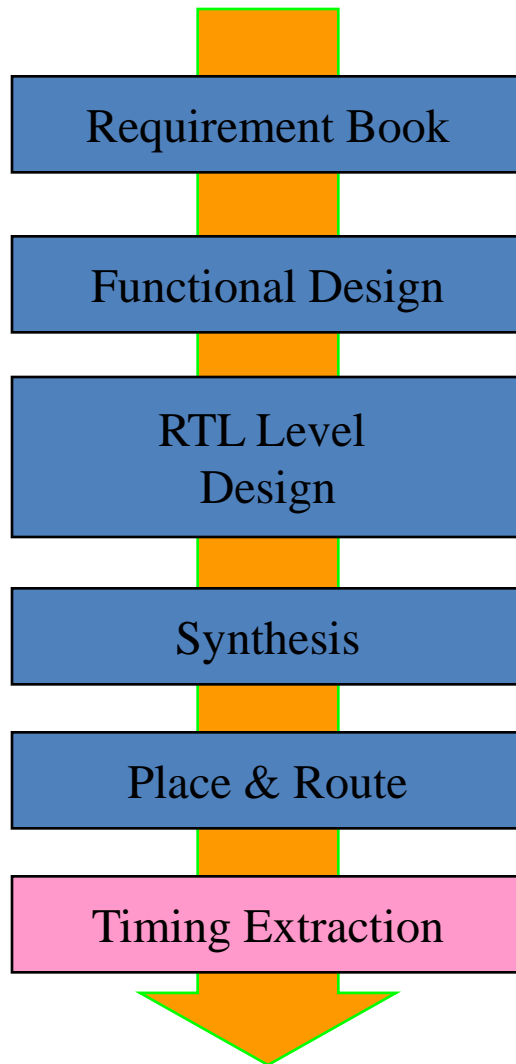


Timing Analyzer Summary

	Type	Slack	Required...	Actual Time	Source Name	Destination Name
1	Clock Setup: 'clock'	985.989 ns	1.00 MHz (...	71.37 MHz (perio...	INS_Decode:D...	ALU:UC_ALU ALUZ
2	Worst-case tsu	N/A	None	11.489 ns	portc[6]	Data_Mux:Dmux A...
3	Worst-case tco	N/A	None	10.414 ns	Spcl_Regs:SP...	portc[5]
4	Worst-case th	N/A	None	-4.776 ns	portb[3]	Data_Mux:Dmux A...
5	Worst-case minimum tco	N/A	None	6.035 ns	Spcl_Regs:SP...	portb[1]

Hardware Implementation

 


Where is the VHDL?

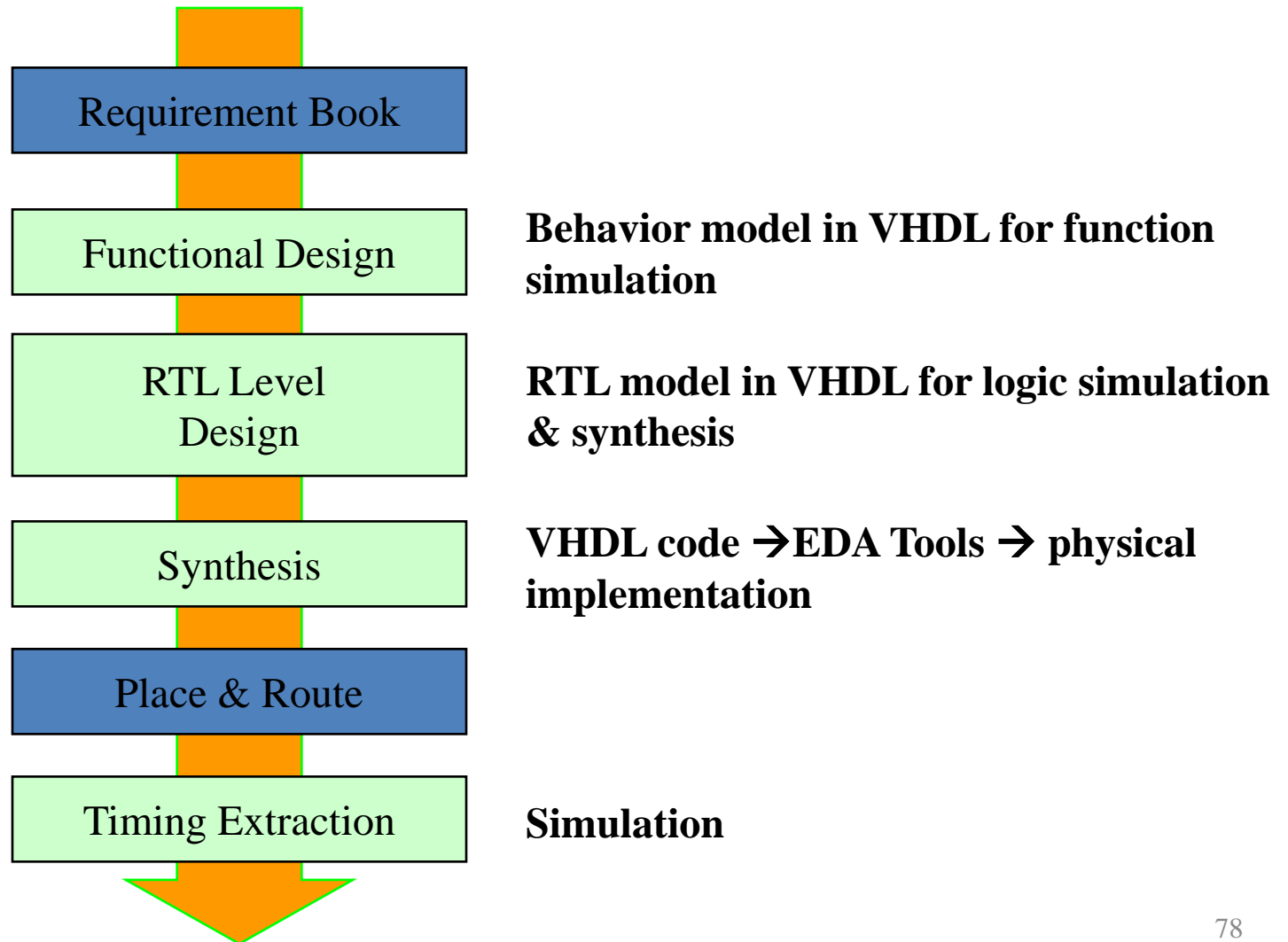

Conclusion

- VHDL is Good
- Describe hardware in different level in digital system design
- Accepted by most EDA tools to help implement digital design
- Help simulating the digital product at different design stage
- Concurrent execution

The Process of Design

 

Design

Initial concept: what is the function performed by the object?

Constraints: How fast? How much area? How much cost?

Refine abstract functional blocks into more concrete realizations

Implementation

Assemble primitives into more complex building blocks

Composition via wiring

Choose among alternatives to improve the design

Debug


Faulty systems: design flaws, composition flaws, component flaws

Design to make debugging easier


Hypothesis formation and troubleshooting skills

Majority Voter Circuit

 - Output '1' if there is more '1's than '0's
- Output '0' if there is more '0's than '1's



Schematic


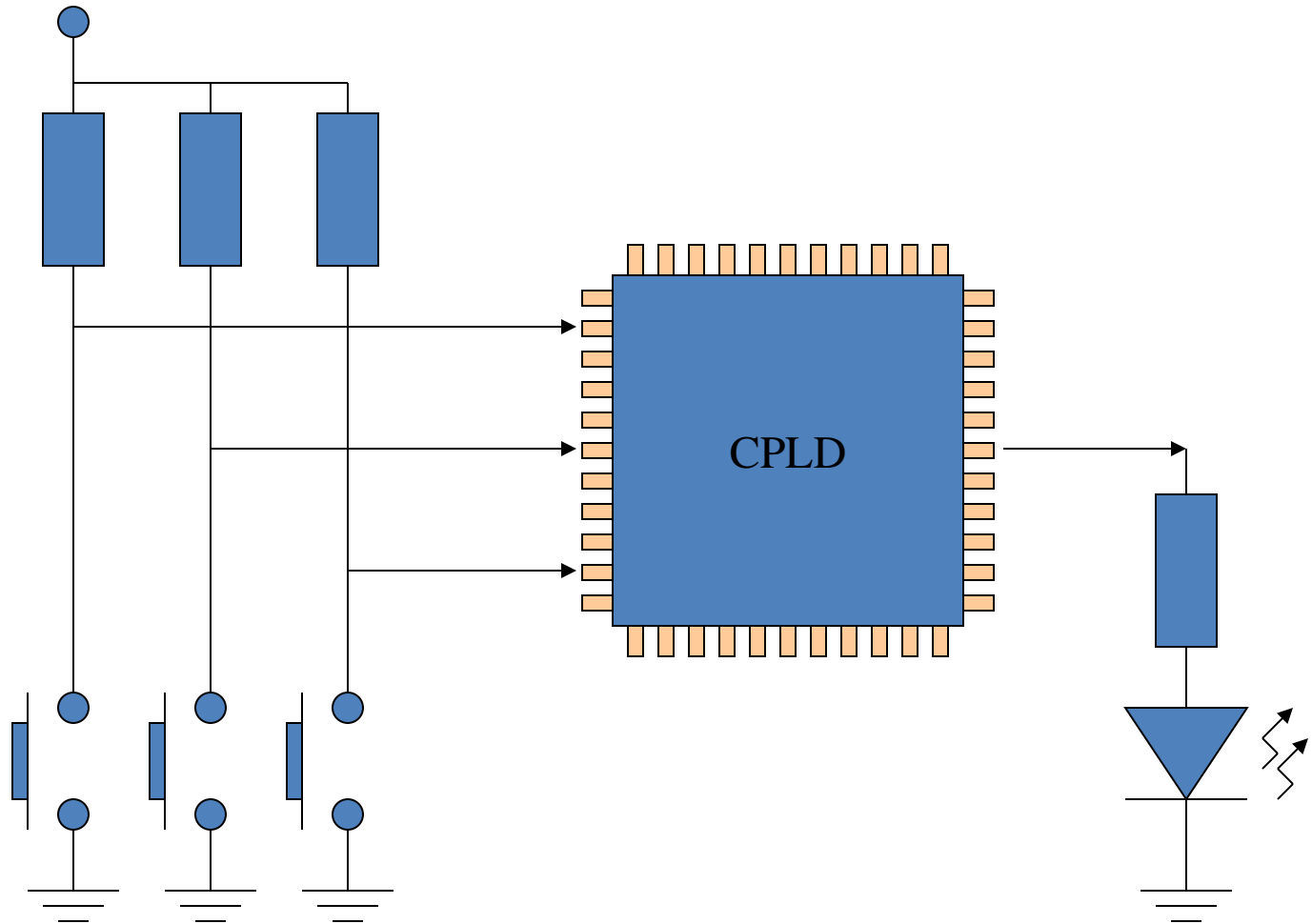


VHDL Description


File

XYZ.VHD

  
- library ieee;
- use ieee.std_logic_1164.all;
- -----
- entity XYZ
- port
- (A1, A2, A3 : in std_logic;
- F : out std_logic);
- end XYZ;
- -----
- architecture XYZ_arch of XYZ is
- begin
- F <= (A1 and A2) or (A2 and A3) or (A1 and A3);
- end XYZ_arch;



Download to Chips

 

XYZ Clock Diagram

 

XYZ.VHD

(1) data flow

- library ieee;
- use ieee.std_logic_1164.all;
- -----
- entity XYZ is
- port
- (
• A, B, C : in std_logic; -- Comments
• F : out std_logic
•);
- end XYZ;
- -----
- architecture XYZ_arch of XYZ is
- begin
- • F <= (A and B) or (B and C) or (C and A);
- • end XYZ_arch;

XYZ.VHD

(2) data flow

- library ieee;
- use ieee.std_logic_1164.all;
- -----
- entity XYZ is
- port
- (
• A, B, C : in std_logic;
- F : out std_logic
-);
- end XYZ;
- -----
- architecture XYZ_arch of XYZ is
- begin
- F <= '1' when ((A = '1') and (B = '1')) else
- '1' when ((B = '1') and (C = '1')) else
- '1' when ((A = '1') and (C = '1')) else
- '0';
- end XYZ_arch;

XYZ.VHD (3) behavioral


- library ieee;
- use ieee.std_logic_1164.all;
- -----
- entity XYZ is
- port
- (
- A, B, C : in std_logic;
- F : out std_logic
-);
- end XYZ;
- -----
- architecture XYZ_arch of XYZ is
- begin
- process (A, B, C)
- begin
- if (A = '1') and (B = '1') then
- F <= '1';
- elsif (B = '1') and (C = '1') then
- F <= '1';
- elsif (A = '1') and (C = '1') then
- F <= '1';
- else
- F <= '0';
- end if;
- end process;
- end XYZ_arch;

XYZ.VHD

(4) structural

```
library ieee;
use ieee.std_logic_1164.all;
library altera;
use altera.maxplus2.ALL;
-----
entity XYZ is
    port
    (
        A, B, C      : in std_logic;
        F            : out std_logic
    );
end XYZ;
-----
architecture XYZ_arch of XYZ is
    signal F1, F2, F3: std_logic;
begin
    U1: and2
        port map(A, C, F1);
    U2: and2
        port map(A, B, F2);
    U3: and2
        port map(B, C, F3);
    F <= F1 or F2 or F3;
end XYZ_arch;
```

XYZ All in One Block Diagram

 

XYZ.VHD

(All in One)

```
library ieee;
use ieee.std_logic_1164.all;
LIBRARY altera;
USE altera.maxplus2.ALL;
--*****
```

```
entity XYZ is
  port
  (
    A, B, C      : in std_logic;
    F            : out std_logic
  );
end XYZ;
--*****
architecture XYZ_arch1 of XYZ is
begin
  F <= (A and B) or (B and C) or (C and A);


end XYZ_arch1;
```

```
architecture XYZ_arch2 of XYZ is
begin
  F <= '1' when ((A = '1') and (B = '1')) else
    '1' when ((B = '1') and (C = '1')) else
    '1' when ((A = '1') and (C = '1')) else
    '0';
```

```
end XYZ_arch2;
-----
architecture XYZ_arch3 of XYZ is
begin
  process (A, B, C)
  begin
    if (A = '1') and (B = '1') then
      F <= '1';
    elsif (B = '1') and (C = '1') then
      F <= '1';
    elsif (A = '1') and (C = '1') then
      F <= '1';
    else
      F <= '0';
    end if;
  end process;
end XYZ_arch3;
-----
```

```
architecture XYZ_arch4 of XYZ
is
  signal F1, F2, F3: std_logic;
begin
  U1: and2
    port map(A, C, F1);
  U2: and2
    port map(A, B, F2);
  U3: and2
    port map(B, C, F3);
  F <= F1 or F2 or F3;
end XYZ_arch4;
-----
```

Expanded Clock Diagram:

 

MY_PACKAGE.VHD

- library ieee;
- use ieee.std_logic_1164.all;
- -----
- package my_package is
- component XYZ is
- port
- (
- A, B, C : in std_logic;
- F : out std_logic
-);
- end component;
- end my_package;

XXYYZZ.VHD

- library ieee;
- use ieee.std_logic_1164.all;
- library work;
- use work.my_package.all;
- -----
- entity XXYYZZ is
- port
- (
- A1, A2, B1, B2, C1, C2 : in std_logic;
- F : out std_logic
-);
- end XXYYZZ;
- -----
- architecture XXYYZZ_arch of XXYYZZ is
- signal F1, F2 : std_logic;
- begin
- G1: XYZ
- port map(A1, B1, C1, F1);
- G2: XYZ
- port map(A2, B2, C2, F2);
-
- F <= F1 or F2;
-
- end XXYYZZ_arch;